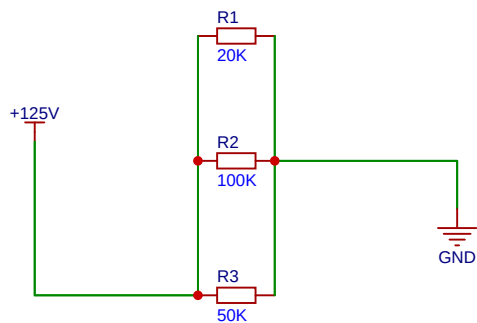




No:	Component:	Value:
1	R1	20
2	R2	100
3	R3	50

Schematic	Schematic2		Create at	2026-05-11
			Update at	2026-05-11
Board			Page	P1
Drawn		Practical Exercise 2: Circuit Design		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com